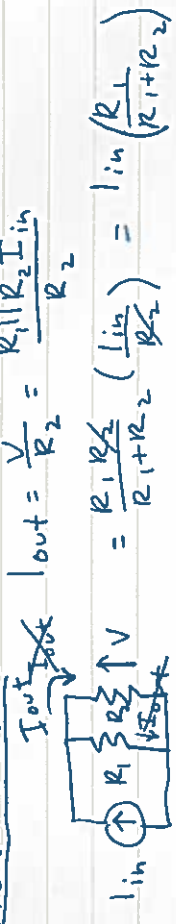




$$V_{out} = V_{in} \left(\frac{R_2}{R_1 + R_2} \right)$$

also ... $V_{out} = IR$
 $= V_{in} - \frac{V_{in}}{R_1 + R_2} (R_1)$

current divider




$$I_{out} = \frac{V}{R_2} = \frac{R_1 I_{in}}{R_2}$$

$$= \frac{R_1 R_2}{R_1 + R_2} \left(\frac{I_{in}}{R_2} \right) = I_{in} \left(\frac{R_1}{R_1 + R_2} \right)$$

Capacitive voltage divider
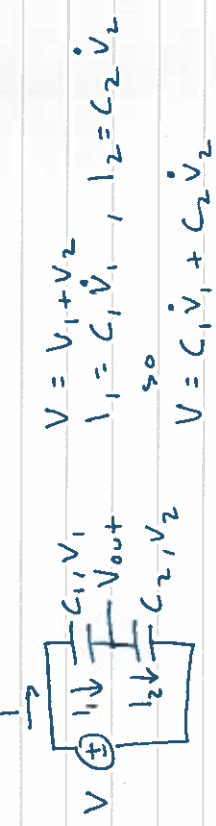
$$Q = CV \quad I = C \dot{V} = \dot{Q} \quad ?? \text{ oh yeah.}$$



$$V_{out} = \frac{I}{C} = \int_0^t \frac{C_1 C_2}{C_2} \cdot V_{in} dt$$

$$V_{out} = \int_0^t (C_1 + C_2) \dot{V} dt = (C_1 + C_2) \frac{dV}{dt}$$



Questions

- nodal analysis? → use laws that apply to nodes (KCL, KVL)
- KCL? → Kirchhoff's current law $I_1 = I_2 + I_3 + \dots + I_n$
- capacitive voltage divider? → $I = (C_1 + C_2 + \dots + C_n) \dot{V}$
- polarized caps. why not use w/ digital voltage?

- a. infinite, parallel
- zero, series


for a current divider:

$$V_{out} = V_{in} \left(\frac{R_2}{R_2 + R_1} \right) \leftarrow \text{"ideal"}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$

$$\Delta \left(\frac{V_{out}}{V_{in}} \right) + \frac{V_{out}}{V_{in}} = \frac{R_2 + \Delta R_2}{R_1 + \Delta R_1 + R_2 + \Delta R_2}$$
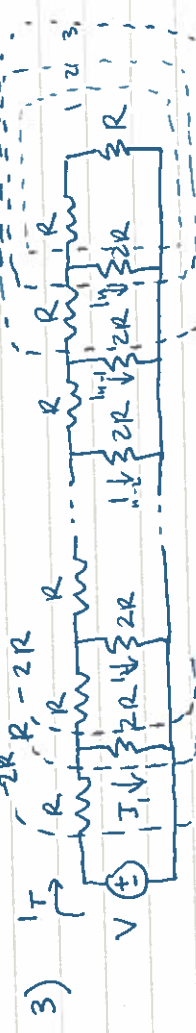
$$\Delta \left(\frac{V_{out}}{V_{in}} \right) = \frac{R_2 + \Delta R_2}{R_1 + \Delta R_1 + R_2 + \Delta R_2} - \frac{R_2}{R_1 + R_2}$$



finding equivalent resistances:

- 1) $2R$
- 2) $2R \parallel 2R \rightarrow \frac{1}{R} = \frac{1}{2R} + \frac{1}{2R} = \frac{2}{2R} = \frac{1}{R}$
- 3) $2R$
- 4) R

so ... $I_T = \frac{V}{2R}, I_1 = I_T/2, I_2 = I_T/2, I_n = I_T/2^n$

4) You can either use 2 resistors in series on the "rungs", or two in parallel on the "sides". Using the former saves you one resistor. Yay!

Ex peripherals

nominal	Keithley
1) R: 280	279.9
$\Delta R: \pm 1\%$	
RR: 1/4 W	