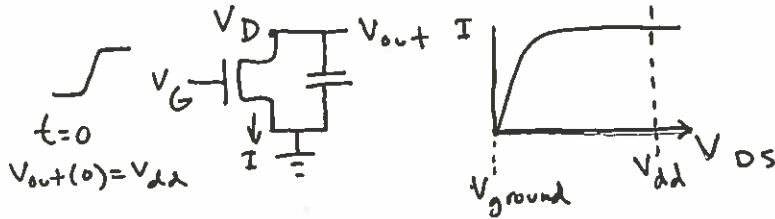


# Postlab 5

Ruby Spring

n MOS  $\left\{ \begin{array}{l} V_G = V_{dd} \rightarrow \text{closed, logic 1} \\ = 0 \rightarrow \text{open, logic 0} \\ \text{strong 0} \end{array} \right.$


p MOS  $\left\{ \begin{array}{l} V_G = V_{dd} \rightarrow \text{open, logic 0} \\ = 0 \rightarrow \text{closed, logic 1} \\ \text{strong 1} \end{array} \right.$



The "capacitor" discharges, and as  $V_{DS} \downarrow$ ,  $V_{GS} \uparrow$  and  $I \downarrow$ .

because  $V_{GS}$  is increasing, the transistor stays on until  $V_D = V_S = V_{ground}$  and no more current can flow ( $I=0$ ).



thus this yields a strong 0

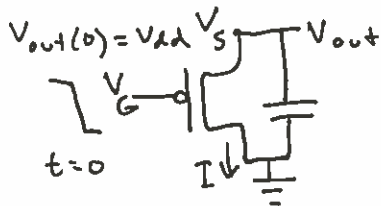



The cap discharges, and as  $V_{DS} \downarrow$ ,  $V_{GS}$  becomes less negative until the transistor turns off and  $I=0$ .

The turn-off occurs before

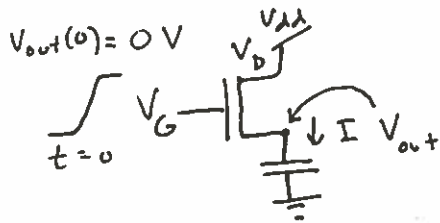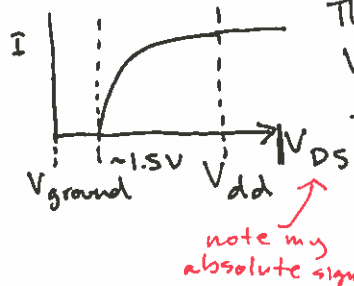$V_G = V_{out}$ , thus we get a  $V_{out} \approx 1.5$  above ground. I'm not entirely sure why it's  $\approx 1.5V$ , I'll try to figure that out ASAP. Thus the transistor can't pull down all the way to zero.



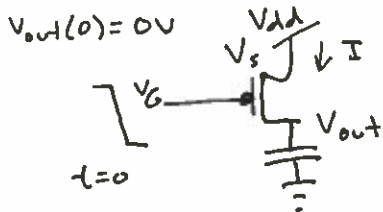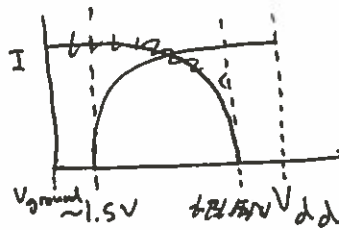The cap charges and as  $V_{DS}$  decreases,  $I \downarrow$  and  $V_{GS} \downarrow$  until  $V_{GS}$  gets too small and the nMOS turns off and  $I \rightarrow 0$ . This occurs about  $1.5V$  below  $V_{dd}$ , thus it is a weak 1



The cap charges and as  $V_{DS} \downarrow$ ,  $I \downarrow$  and  $V_{GS}$  becomes more negative, keeping the transistor on until  $V_{out} = V_{dd}$ . Thus this is a strong 1

