

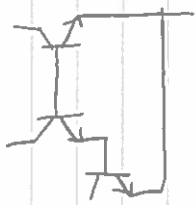
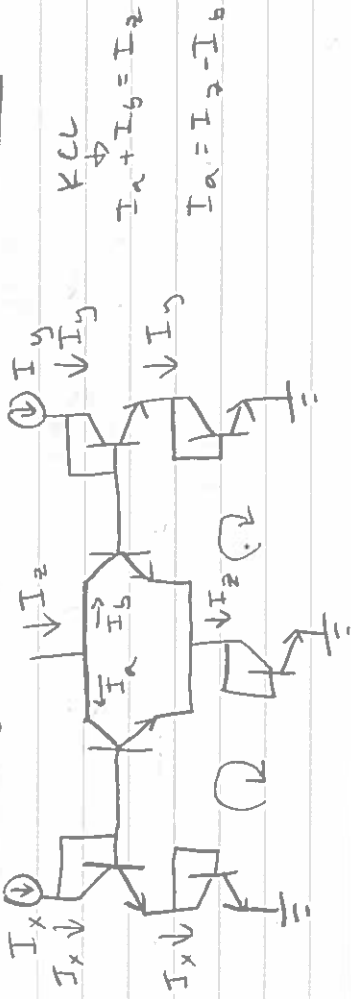


if loop not symmetrical:

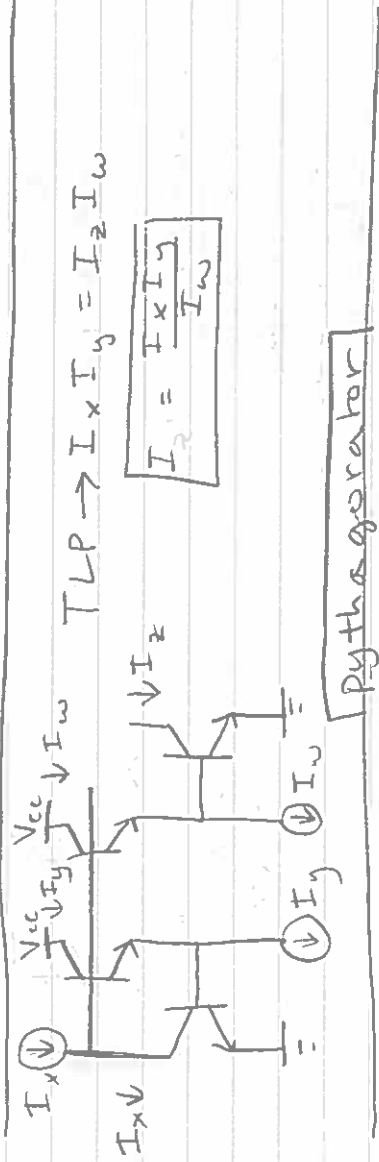

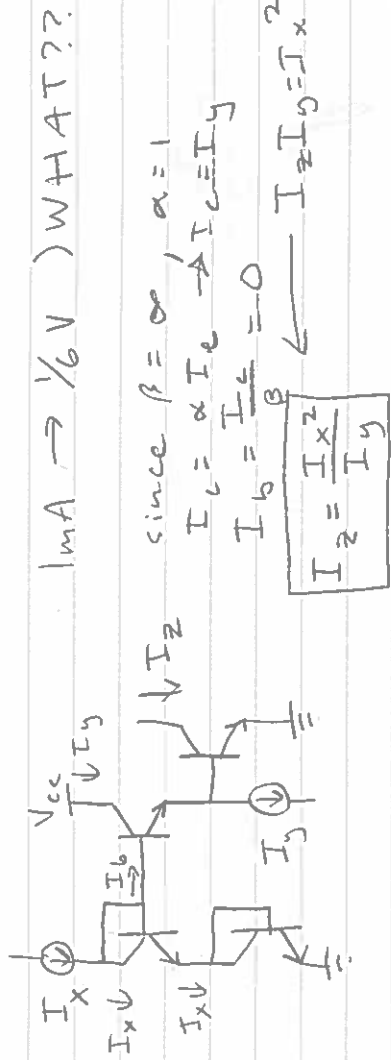
$I_1, I_2 = I_3(I_5)$  ← varies drastically w/ temp, don't design circuits that depend on  $I_5$ !



$TLP \rightarrow I_x^2 = I_a I_z$   
 $I_a = \frac{I_x^2}{I_z}$   
 $I_z = I_a + I_b = \frac{I_x^2 + I_y^2}{I_z}$   
 $I_z^2 = \sqrt{I_x^2 + I_y^2}$

## Postlab 3

Ruby Spring

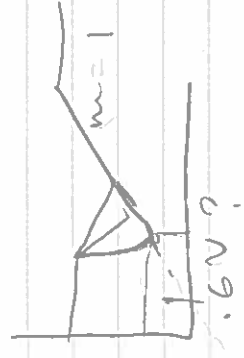

The voltage at the collector,  $V_{out}$ , is determined by

$$V_{out} = V_{cc} - I_m R$$

So we see it is affected by the collector current,  $I_c$ .

As  $V_{in}$  increases, the BJT eventually reaches deep saturation where the collector-base junction is reverse-biased. and some current begins to flow the opposite direction (from the base to the collector), thus decreasing  $I_c$ . This decrease in  $I_c$  leads to a decrease in  $V_{out}$ . Why the slopes are all unity, I have yet to figure out, but I think, because they all overlap perfectly with the data from experiment 2, it has something to do with the emitter resistor value.