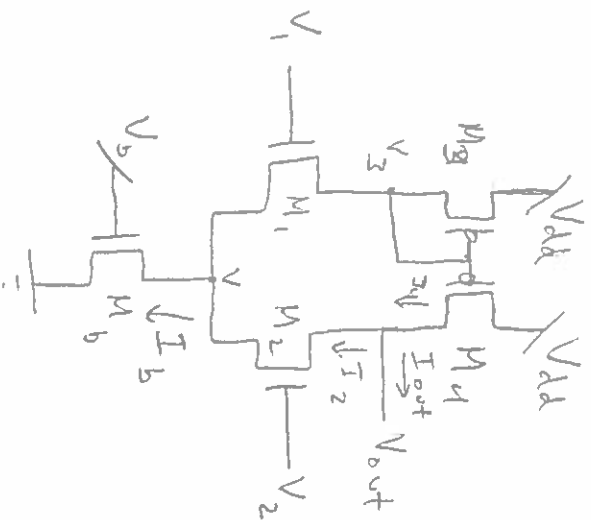


①



KCL \rightarrow

$$I_{out} = I_{q1} - I_{q2}$$

im not sure if that's the
kindly answer you were
looking for...

② If we let go of V_{out} :

if I_{out} is positive, V_{out} goes up
" " negative, " " down
" " zero, " " nowhere

③

if $V_1 \uparrow, V_2 \downarrow \rightarrow I_{q1} \uparrow \rightarrow I_{out} \uparrow$
so V_1 is the noninverting input

if $V_2 \uparrow, I_2 \uparrow \rightarrow I_{out} \downarrow$

so V_2 is the inverting input

④

a) if $V_1 = V_2$ ($= V_{cm}$) $\rightarrow I_1 = I_2 \rightarrow I_{out} = 0$

b) if $V_{cm} = \frac{1}{2}(V_1 + V_2) \uparrow$, so long as $V_1 = V_2$ $I_{out} = 0$

c) under these circumstances, $A_{cm} \approx \frac{\delta V_{out}}{\delta V_{cm}} = 0$ b/c $\delta V_{out} = 0$

d) if $V_{dm} = V_1 - V_2 \uparrow$, then $V_1 > V_2$ and $I_{out} \uparrow$

e) if V_{out} is drawing no current, $V_{out} = V_3$

f) if $V_{dm} \downarrow$, then $V_2 > V_1$, and $V_{out} \uparrow \leftarrow$ if V_{out} is connected to a voltage source so current can flow

g) $A_{dm} \approx \frac{\delta V_{out}}{\delta V_{dm}} \approx$ really big b/c δV_{dm} is very small compared to δV_{out}